Assignment

Course Name: Digital Logic Design

Course Code: CSE 345

Section No:2

Title: Design a 2 bit full subtractor circuit using suitable multiplexer and simulation.

Submission date: -

Date of experiment: -

Submitted To:

Dr. Md Sawkat Ali
Associate Professor
Department of Computer Science and Engineering

Submitted by:

Name	ID
1.Ratul Hasan Nirjon	2023-3-60-498